




# Boolean Algebra Worksheet


1. Write the Boolean expression underneath each symbol:



$Q =$

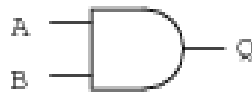


$Q =$

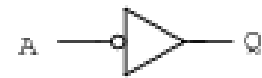


$Q =$




$Q =$

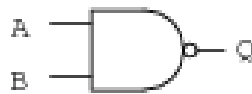

$Q =$

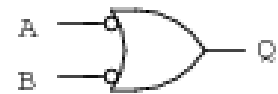




$Q =$

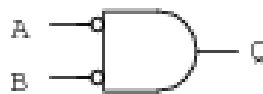

$Q =$


Look at these two simple logic circuits. Are they equivalent? Does it matter where the NOT gates occur?

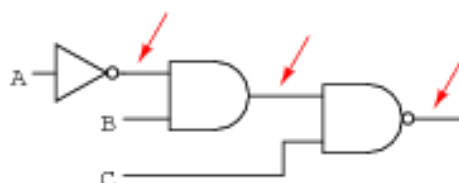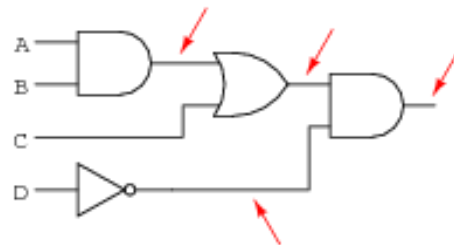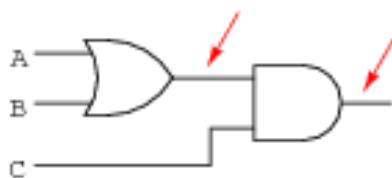2. Convert each logic circuit into a Boolean expression, writing each gate's output next to the arrows:





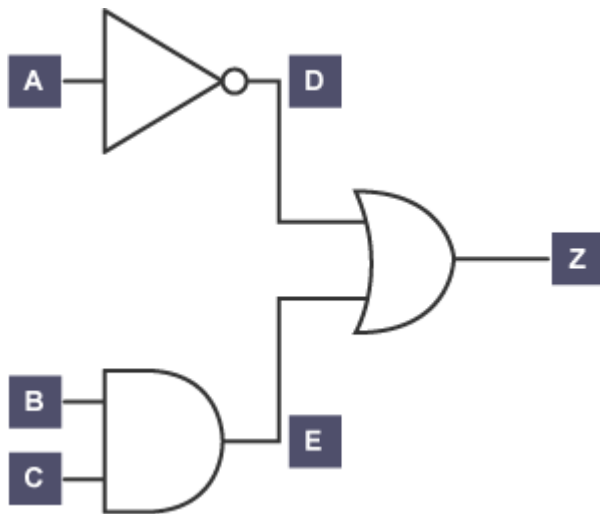3. Complete the truth table for the following logic circuit:



A	B	C	D=¬A	E=BC	Z=D+E
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

4. Write the final Boolean expression (Z) for the above diagram using the inputs A, B and C in your answer.

**Boolean Algebra Expression Symbols Reference:**

Logic Gate	Boolean Symbol	Examples of Use
AND	·	$A \cdot B$ (common)
	x	$A \times B$
	*	$A * B$
	v	$A \vee B$
	[no gap or symbol]	$AB$ (common)
OR	+	$A + B$ (common)
	^	$A \wedge B$
XOR	⊕	$A \oplus B$
NOT	—	$\overline{A}$ (common)
	!	$!A$
	¬	$\neg A$
	'	$A'$